



## Understanding the Smith Chart

### Introduction

The Smith chart is a useful graphical tool to convert between impedances and reflection coefficients. It may also be used to solve impedance-matching problems. It can be thought of as a polar reflection coefficient chart with overlaid impedance curves.

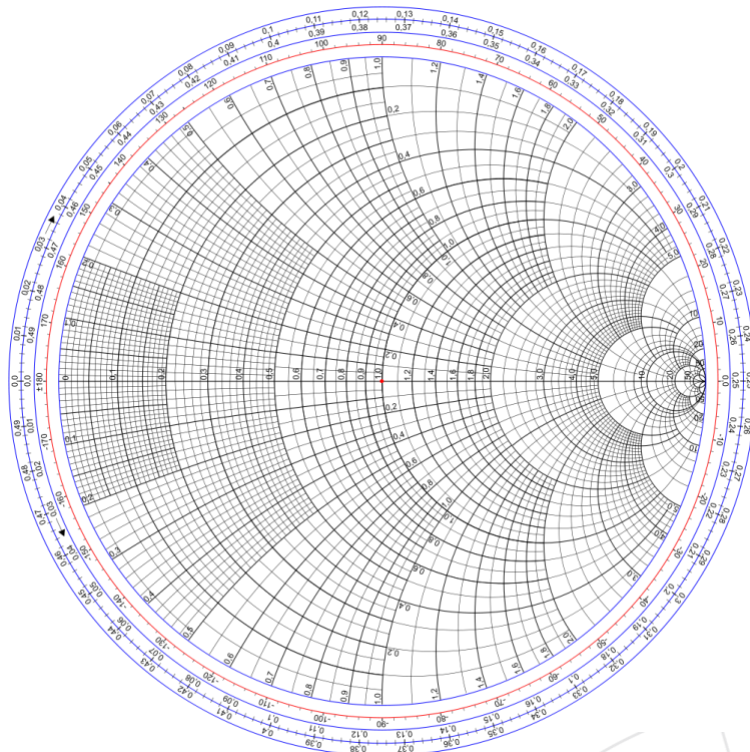


Figure 1 - Smith Chart

### Reflection Coefficients

The reflection coefficient of an impedance can be measured with a vector network analyzer.

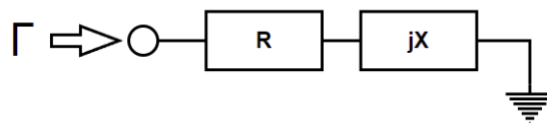


Figure 2 – Measured Reflection Coefficient





## Understanding the Smith Chart

That reflection coefficient will be:

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

Equation 1 - Reflection Coefficient

where  $Z$  is the complex impedance  $R+jX$  and  $Z_0$  is the characteristic impedance of the source.

For  $Z = Z_0$ , the reflection has a magnitude of zero, a dot at the center of the smith chart.

For  $Z = 0$ , the reflection is  $1\angle 0$  or Cartesian  $1,0$ .

For  $Z = \infty$ , the reflection is  $1\angle 180$  or Cartesian  $-1,0$ .

For  $Z = 23+j75$ , the reflection coefficient is  $0.762\angle 64$  or  $0.333+j0.685$

These four reflections are plotted on the polar plot in Figure 3.

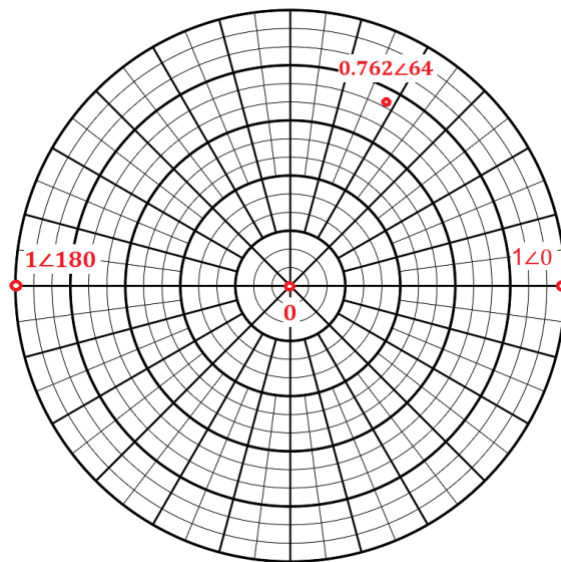


Figure 3 - Polar Reflection Coefficients





## Understanding the Smith Chart

### Building the Smith Chart

These reflection coefficients were calculated from Equation 1. Using this equation, we could choose a real part of the impedance, the resistance, hold it constant, and then let the imaginary part, the reactance, go from  $-\infty$  to  $+\infty$  and draw the result on the polar plot.

With the resistances normalized to 50 ohms, we can draw these circles of constant resistance for 10, 20, 50, 100, and 200 ohms, or 0.2, 0.4, 1, 2, and 4 when normalized.

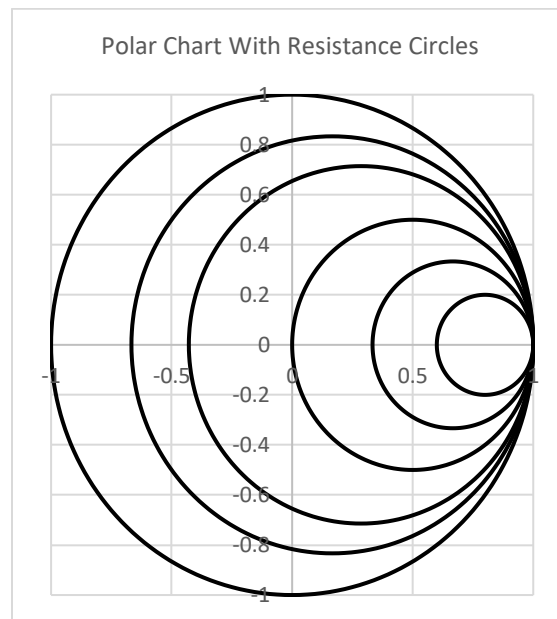


Figure 4 - Polar Chart with Resistance Circles

The circles are centered at  $R/(R+1), 0$ , with a radius of  $1/(R+1)$ , where  $R$  is the normalized value.

We can then choose reactances and sweep the resistance from  $-\infty$  to  $+\infty$  to obtain arcs of constant reactance.



## Understanding the Smith Chart

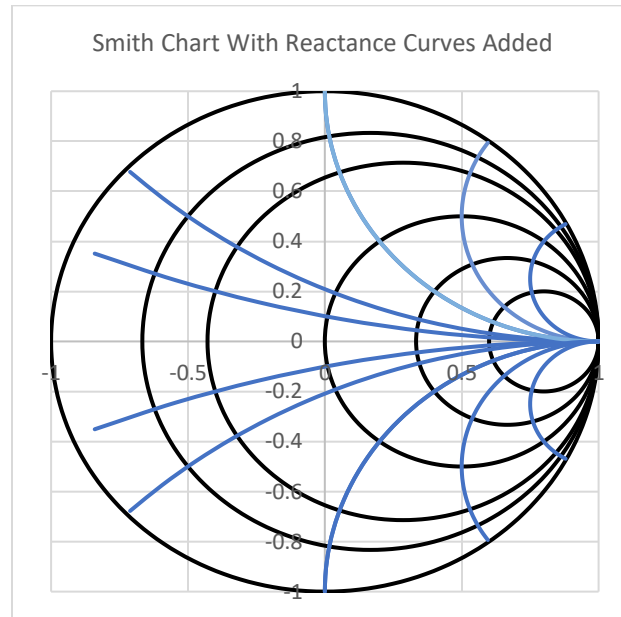


Figure 5 - Completed Smith Chart

After the circles of resistance and curves of reactance are added to the polar chart and labeled, one can locate the reflection coefficient of any impedance by inspection.

### Impedance Matching

You can use a Smith chart to assist in impedance matching with lumped elements or transmission lines. For instance, if we start at an impedance of  $20 + j35 \Omega$  and want to match to  $50 \Omega$  at 500 MHz, we can use a shunt capacitor followed by a series capacitor. To make the graphical method simpler, a mirror image of the resistance and reactance circles and arcs must be added (in blue in Figure 6) to represent shunt conductance and susceptance.

The first step is to add a shunt term to provide enough susceptance to get to the constant  $50 \Omega$  resistance circle. To get from  $20 + j35$  to the constant  $50 \Omega$  resistance circle, we added  $11.9 \times 10^{-3}$  mhos of capacitive susceptance, or  $3.8 \text{ pF}$  at 500 MHz. From there, a negative reactance of  $39.8 \text{ ohms}$  is needed to get to the center of the Smith chart, or  $8.0 \text{ pF}$  at 500 MHz. These manipulations can be done directly on a Smith chart, but it is much simpler to use the Smith program designed by Prof. Fritz Dellsperger at [www.fritz.dellsperger.net](http://www.fritz.dellsperger.net). The demo version is free of charge, while the licensed version has more features. It is very instructive to see how the addition of series or shunt elements moves the chart's impedance.



## Understanding the Smith Chart

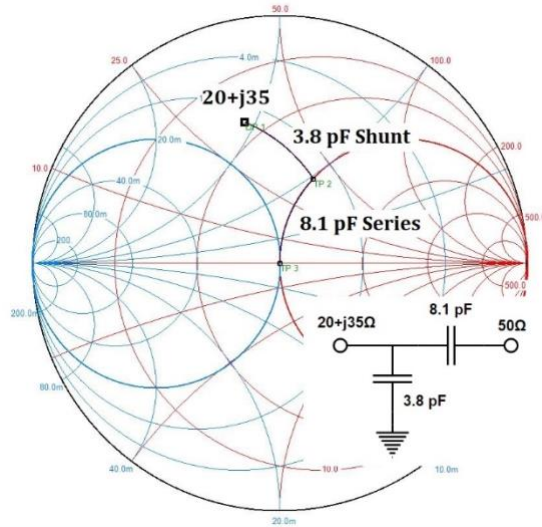


Figure 6 – Matching

This same match could be accomplished with a series capacitor to get to the  $0.02\text{ mho}$  conductance circle ( $1/50\Omega$ ), followed by a shunt capacitor to get to the middle of the Smith chart.  $30.1\text{ pF}$  and  $7.8\text{ pF}$  respectively, as in Figure 7.

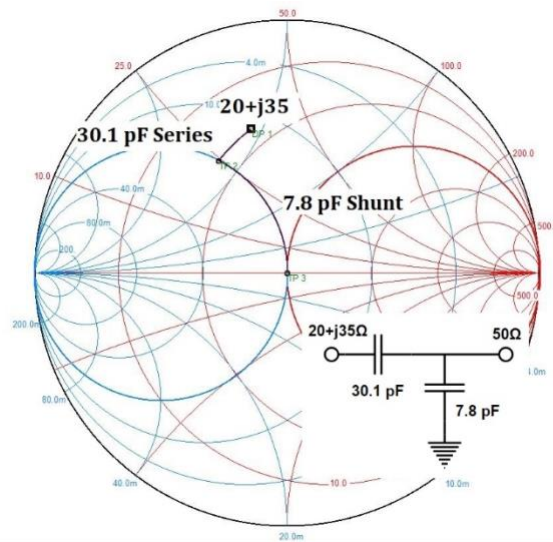


Figure 7 - Alternate Match





## Understanding the Smith Chart

Finally, you could use a 5.3 pF series capacitor to get to the 0.02 m-mho ( $1/50\Omega$ ) conductance circle on the other side, and then use a shunt 13 nH inductor, as in Figure 8, to get to the middle of the Smith Chart. The possibilities are endless, but the matching bandwidth will become narrower and narrower as more distance is traversed on the chart.

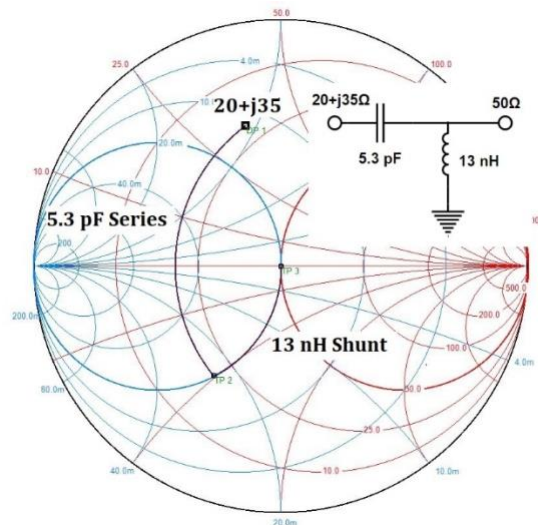


Figure 8 - LC Match

### Transmission Line Matching

Transmission lines can also be used for impedance matching. In a special case, if it is necessary to match from one real impedance to another, such as  $50\Omega$  to  $100\Omega$ , a quarter wavelength transmission line with impedance of the square root of the product of the two, or  $70.7\Omega$  will work.



## Understanding the Smith Chart

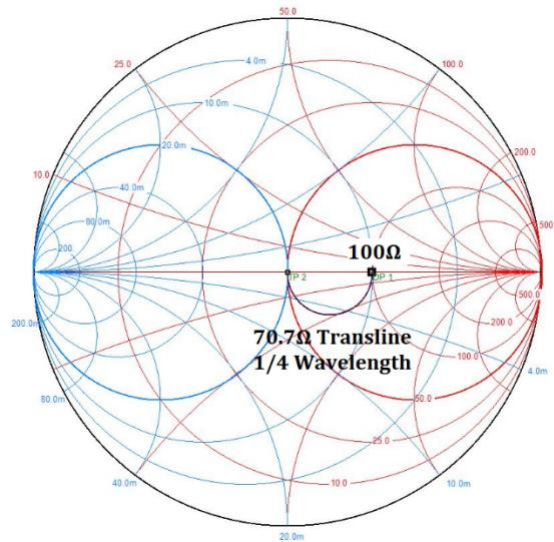


Figure 9 - Series Transmission Line Match

A Wilkinson power splitter is comprised of two, quarter wavelength  $70.7\Omega$  transmission lines, which are joined together at one end. Each  $50\Omega$  terminated line looks like  $100\Omega$  where they are joined together, resulting in an effective  $50\Omega$  impedance.

In general, a series transmission line will rotate any real impedance  $Z$  clockwise around impedance  $\sqrt{Z} * 50$  and a  $50\Omega$  transmission line will rotate an impedance around the center of the Smith chart.

For a large change in impedance, such as from  $50\Omega$  to a  $2\Omega$  LDMOS power amplifier gate, make the transition in two or more steps to maximize the match bandwidth. A quarter wavelength  $6\Omega$  line, followed by a quarter wavelength  $30\Omega$  line, is preferable to a single quarter wavelength  $10\Omega$  line. The bandwidth is superior, as shown in Figure 11.



## Understanding the Smith Chart

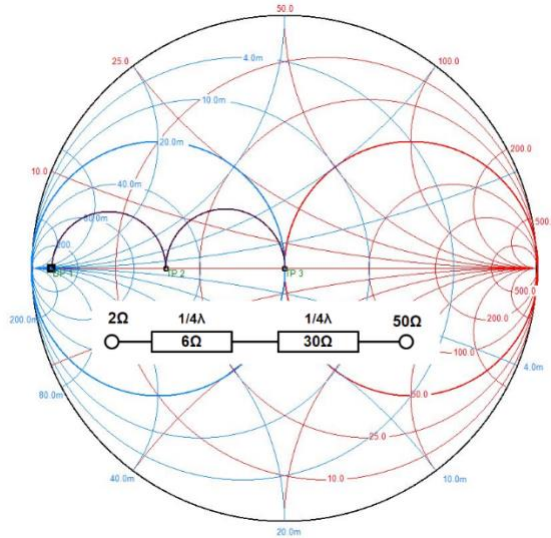


Figure 10 - Transmission Line Match

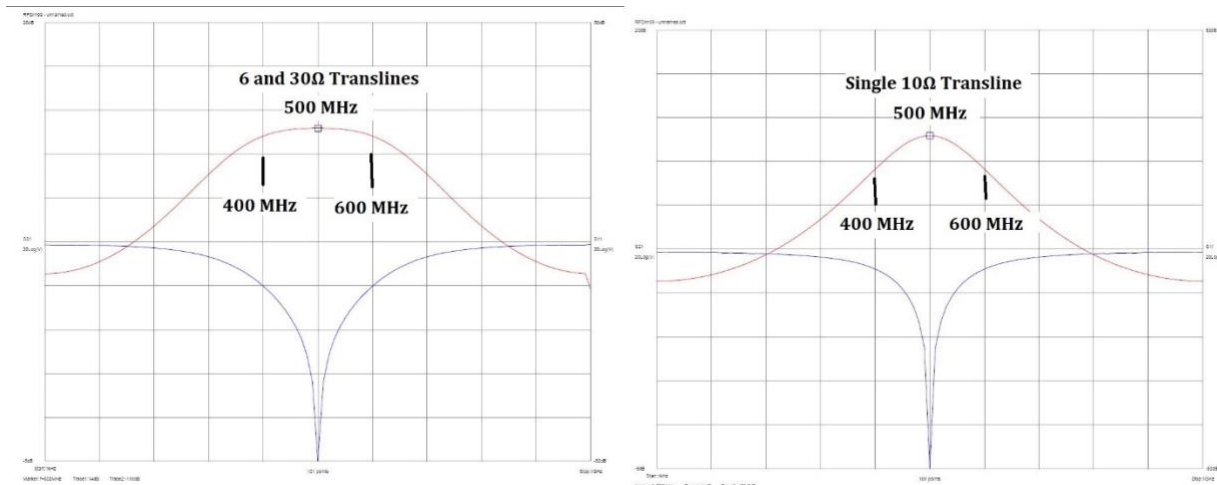


Figure 11- Two vs One Transmission Line Match





---

## Understanding the Smith Chart

---

### Summary

The Smith chart is a very convenient tool to graphically calculate and visualize impedance transformations with lumped elements or transmission lines. There are many lumped element solutions for any given matching problem, and transmission lines—particularly quarter wavelength lines— may be used singly or in cascade to match two real impedances.

The chart is educational and helps provide an intuitive understanding of impedance transformations.